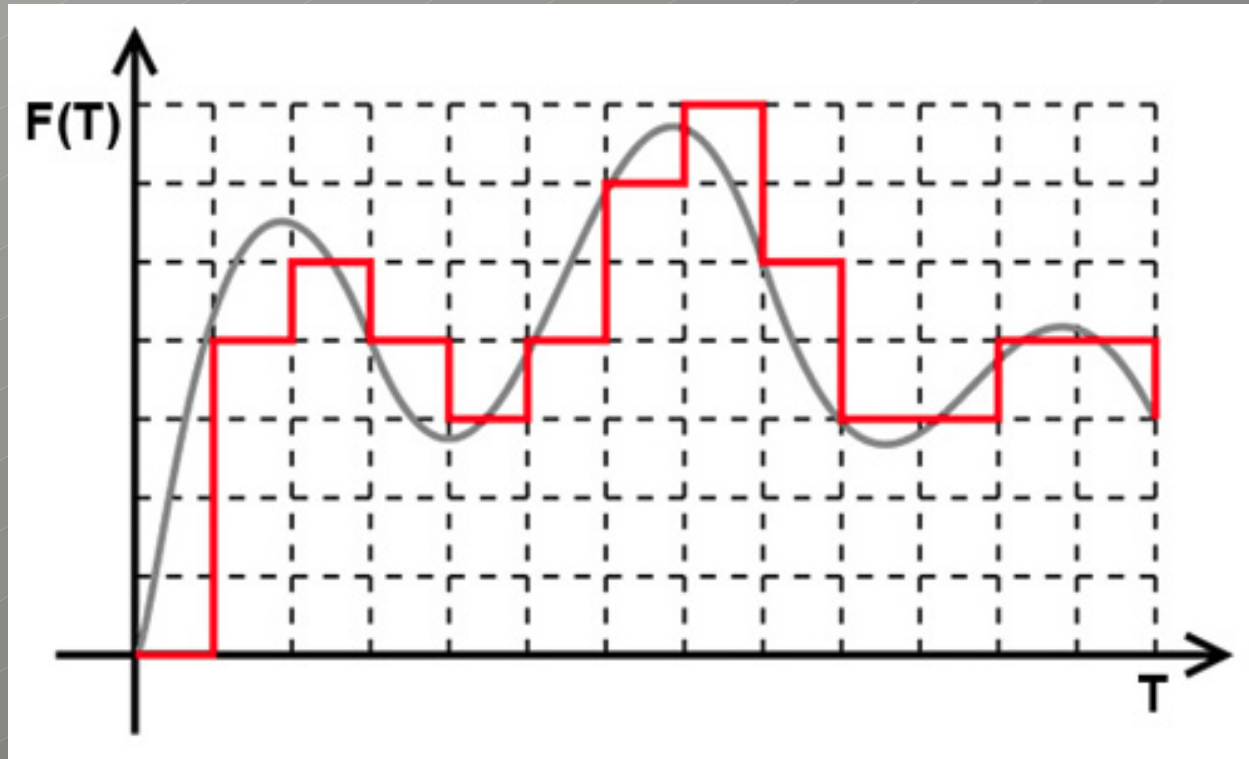


Analog To Digital Converter




Content

- What is an ADC? (recap)
- Different types of ADCs
- Atmel SAM ADC
- Working example
- Practical considerations

What is an ADC?

- Digital interface to the analog world
 - Approximation of a (true) analog signal
 - Discretization of a continuous time signal
- ADCs are used for
 - Control/Scientific applications
 - Digital Signal Processing
 - Audio (and Video) recording
 - ...

What is an ADC?

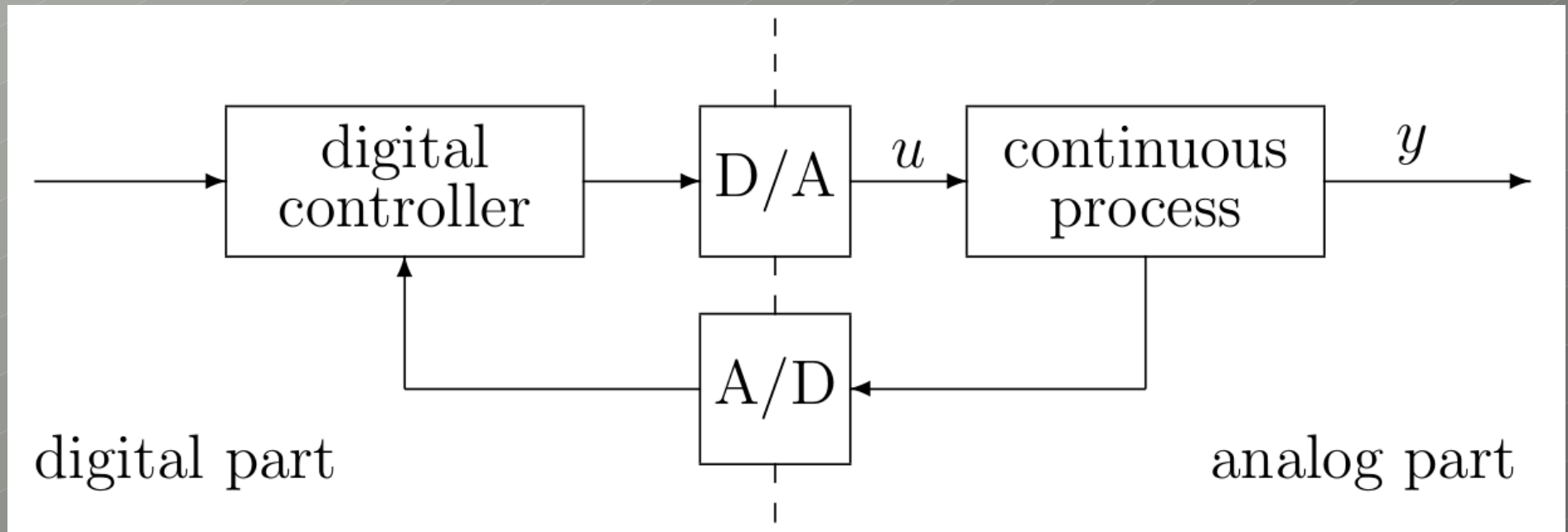


What is an ADC?

- Different ADC differ in many aspects
 - Accuracy
 - Voltage Reference
 - Resolution
 - Sampling Rate
 - Input range
 - Input mode (eg. single ended or differential)


Different Types of ADCs

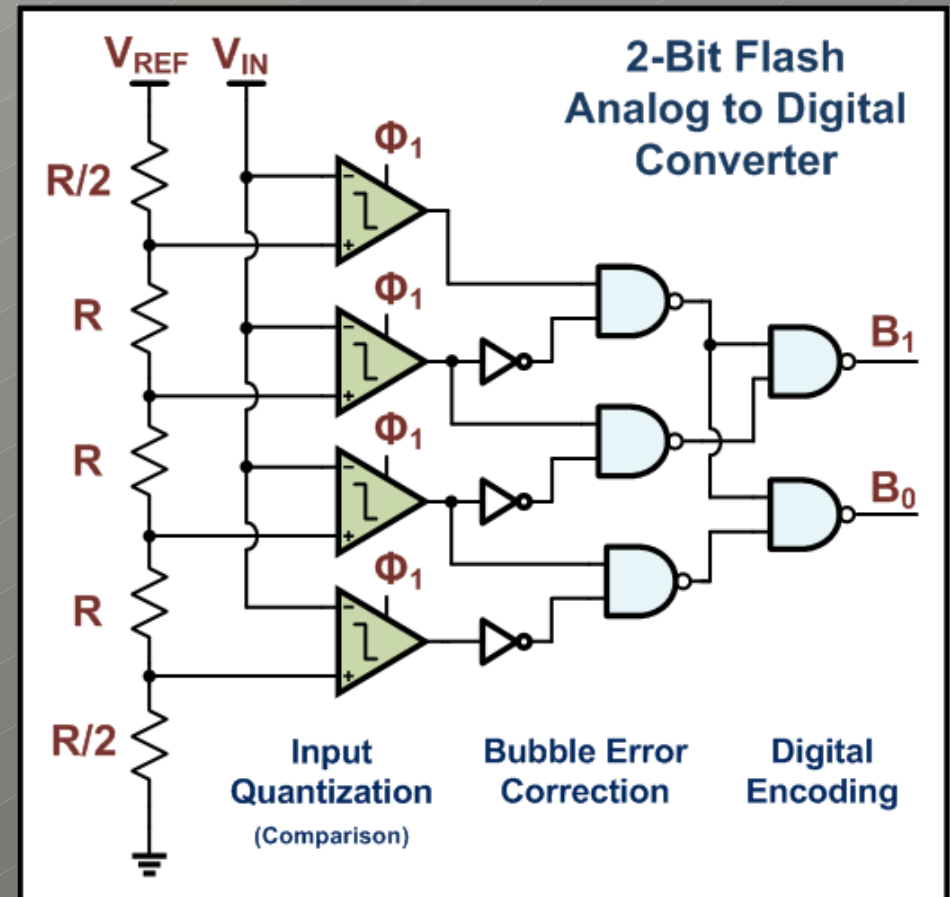- Flash ADC
 - Extremely fast
 - Quiet simple
 - Requires logic circuitry only
 - Huge number of comparators
 - Increased power consumption





Different Types of ADCs

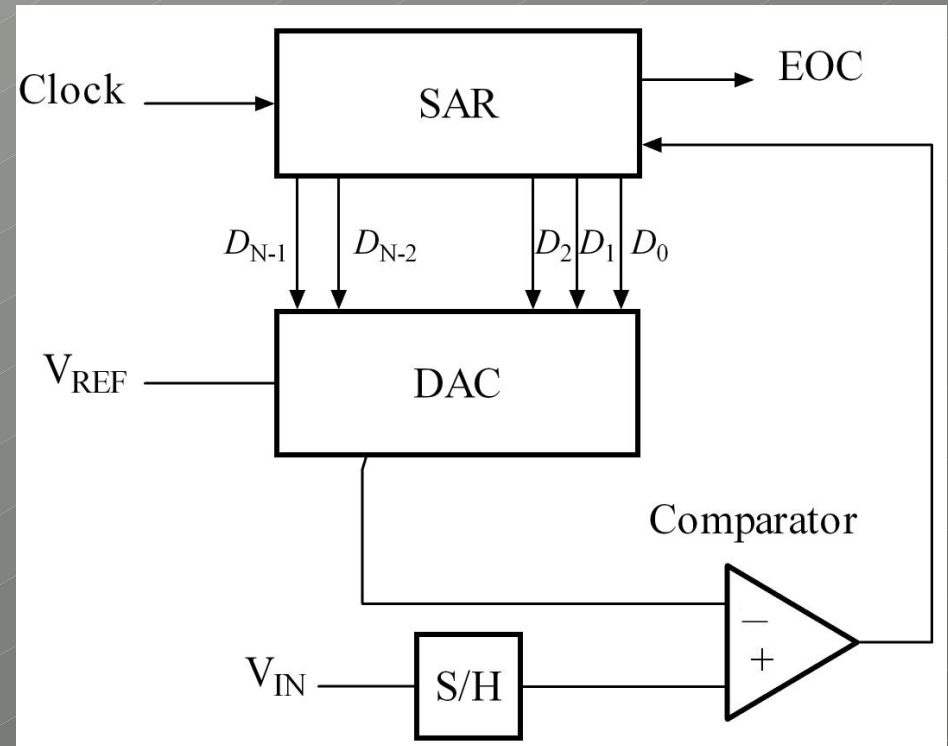- SAR
 - Digital approximation via binary search
 - Popular for multi channel applications
 - Error can exceed multiple bits



Different Types of ADCs

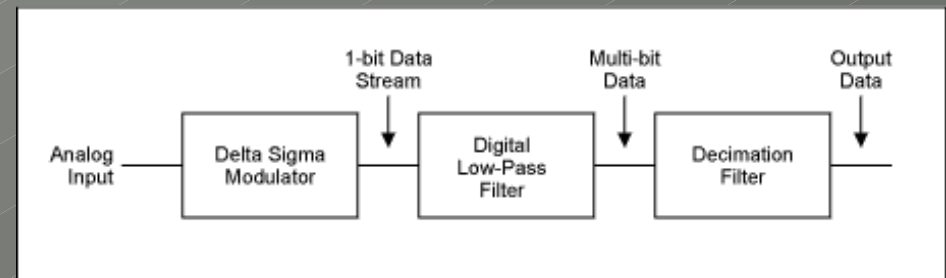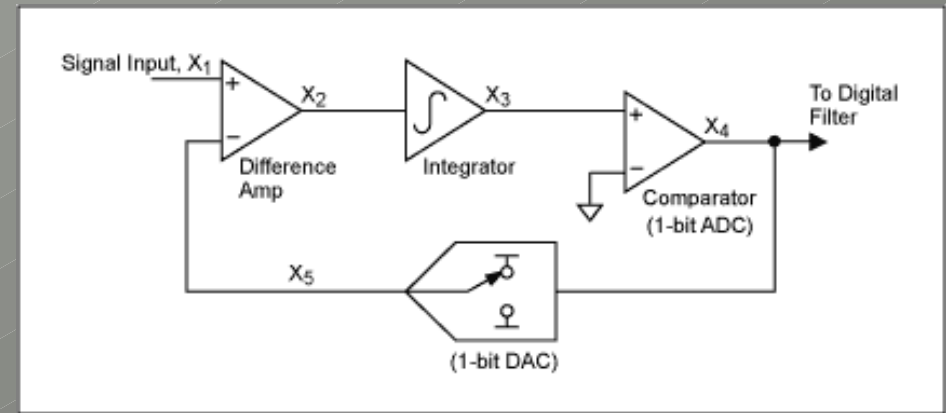- Delta Sigma
 - 1 bit Analog ADC
 - More complex digital side
 - Noise shaping by DAC
 -




Differnt Types of ADCs

- And many more...
 - Ramp compare
 - Wilkinson
 - Integrating ADC
 - Delta Encoded
 - Pipeline
 - ...

Atmel SAM ADC

- Selectable 8, 10 or 12 bit resolution
 - 16 bit in oversampling
- 350 ksps (thousand samples per second)
- Averaging feature
- Differential and Single Ended inputs
- Built in and external Vref options
- Selectable Gain

Atmel SAM ADC

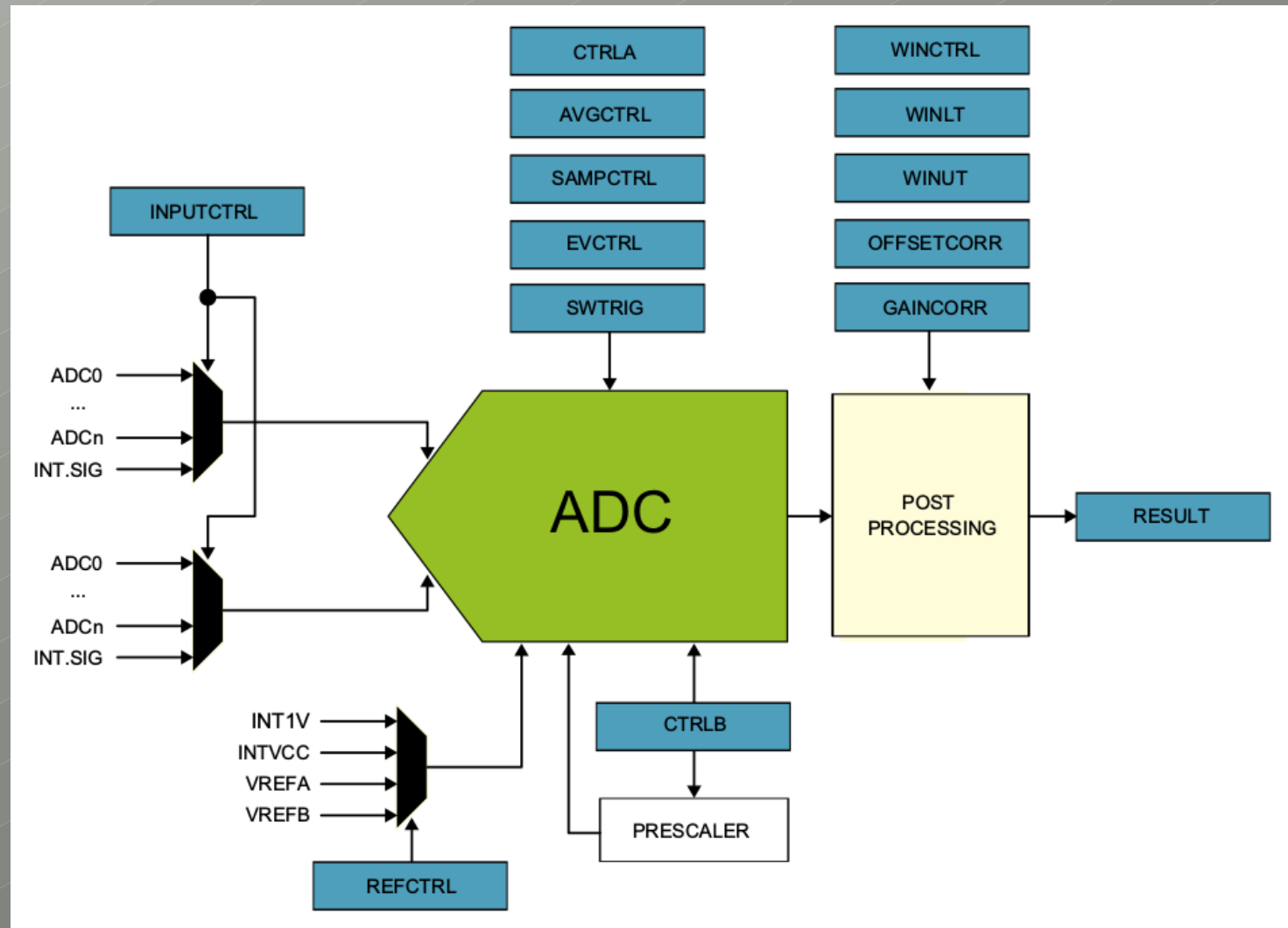


Working Example

<C++>


Practical Considerations

- Use internal or external ADC may depend on application and performance
- Sample rate and accuracy are crucial for control systems application
 - Always consider aspects of discretization (!!!)
- Consider the maximal bandwidth of your circuit
 - Nyquist frequency (anti aliasing filters)
 - Analog signal processing


Practical Considerations

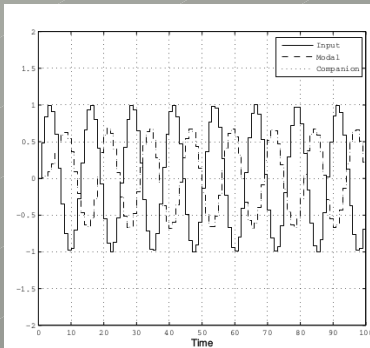


(a) $T_s = 1s$, 32bit

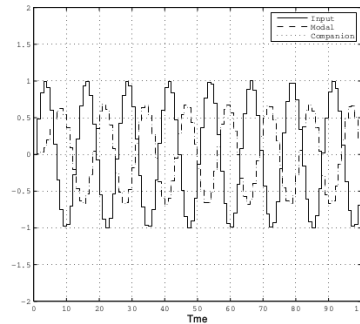


(b) $T_s = 1s$, 16bit

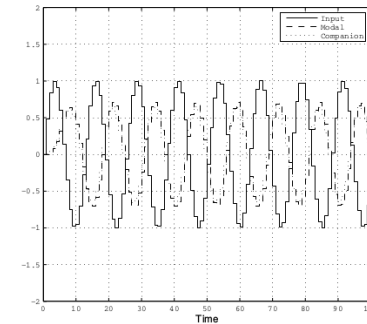


(c) $T_s = 1s$, 8bit

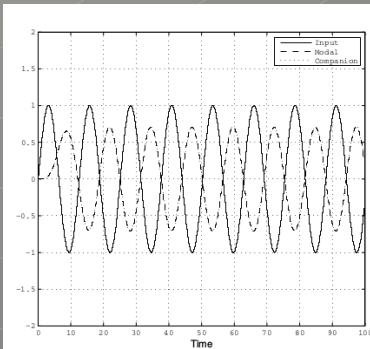

(a) $T_s = 0.1s$, 32bit

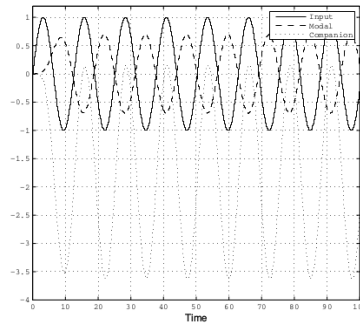

(b) $T_s = 0.1s$, 16bit

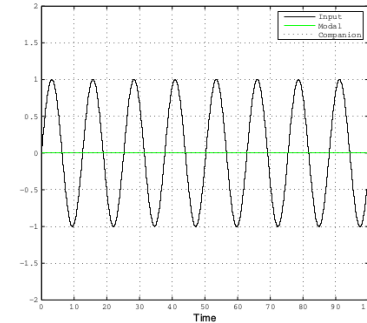

(c) $T_s = 0.1s$, 8bit

Useful Links

- <http://www.analog.com/en/analog-dialogue/articles/the-right-adc-architecture.html>
- <http://www.hardwaresecrets.com/how-analog-to-digital-converter-adc-works/>
- <https://www.maximintegrated.com/en/app-notes/index.mvp/id/1870>